

Module 3: Lab1

1 DESIGN

Our Design in this Lab is a simpler arbiter.

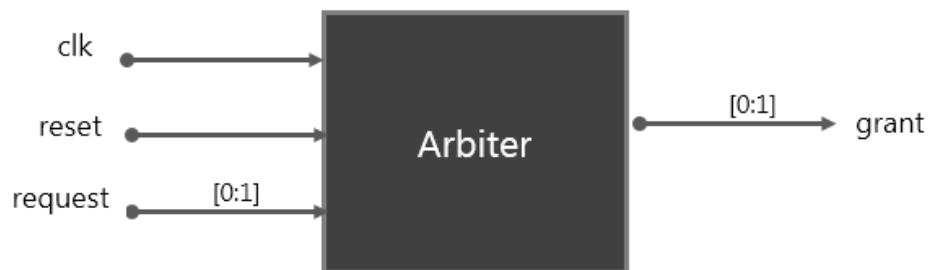


Figure1: Arbiter DUT

Request	Grant (next clock cycle)
2'b00	2'b00
2'b01	2'b01
2'b10	2'b10
2'b11	2'b11
At reset grant is 2'b00	

Figure2: Truth Table for DUT functionality

2 TESTBENCH

A simple testbench has been provided. The test bench sends random transactions in and checks the output using a golden reference model.


 


Figure3: Integrate Testbench and Arbiter

3 LAB EXERCISE

 1. Write a top level file to integrate the testbench and Arbiter. The clock should be generated in the top level file and passed to the Testbench and the Arbiter.



2. Is there a bug in the design?